

Course Name:	Elements of Electrical and Electronics Engineering	Semester:	I/II
Date of Performance:		Batch No:	G3
Faculty Name:	Milind Marathe	Roll No:	16010421063
Faculty Sign & Date:		Grade/Marks :	/ 25


Experiment No: 9

Title: Measurement of Power using Two Wattmeter Method

Aim and Objective of the Experiment:
<ul style="list-style-type: none"> To measure the power of three phase power using Two Wattmeter Method

COs to be achieved:
CO1: Analyze resistive networks excited by DC sources using various network theorems.

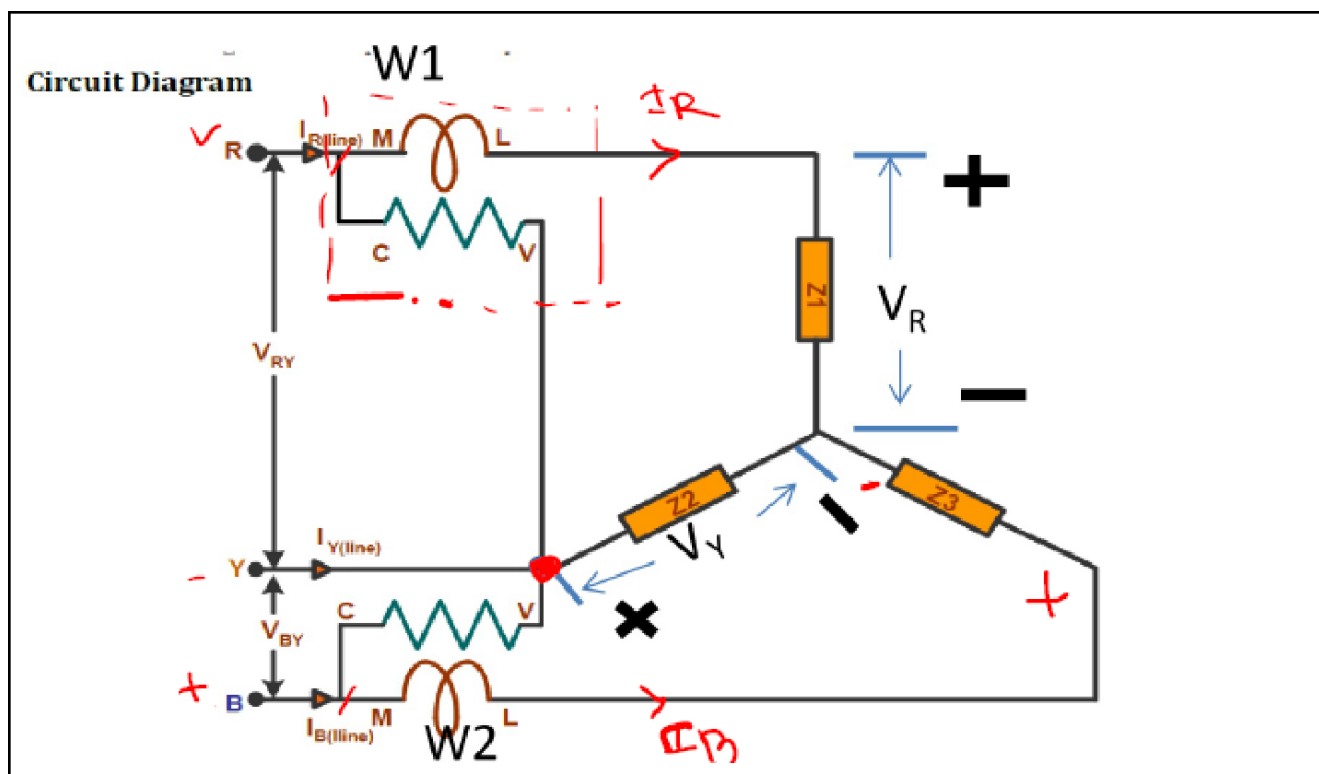Circuit Diagram/ Block Diagram:
Circuit Diagram



Stepwise-Procedure:

1. Connect the circuit as shown in circuit diagram
2. Increase the load and note down the reading V_L , I_L , W_1 and W_2
3. Practically you will obtain total power $W = W_1 + W_2$
4. Theoretically power is measured by using formula $P = \sqrt{3} V_L I_L \cos \phi$, using $\cos \phi = 1$ (unity) for resistive load.

Observation Table:



STAR LOAD




Sr No.	Load	V_L	I_L	W_1	W_2	$W = W_1 + W_2$	$\sqrt{3} V_L I_L \cos \phi$
1	$R = 100$	398 V	2.28 A	791 W	793 W	1584 W	1571.68 W
2	$R = 100$ $L = 1H$	398 V	0.70 A	-59.4 W	205 W	145.6 W	146.36 W
3	$R = 100$ $C = 10\mu F$	398 V	0.69 A	201 W	60 W	261 W	260.69 W


DELTA LOAD

Sr No.	Load	V_L	I_L	W_1	W_2	$W=W_1+W_2$	$\sqrt{3}V_L I_L \cos\phi$
1	$R = 100$	395 V	6.89 A	2370 W	2380 W	4750 W	4713.72 W
2	$R = 100$ $L = 1H$	395 V	2.1 A	-178 W	614 W	436 W	428.36 W
3	$R = 100$ $C = 10\mu F$	395 V	2.06 A	605 W	-179 W	426 W	415.78 W

Screenshot of Output:

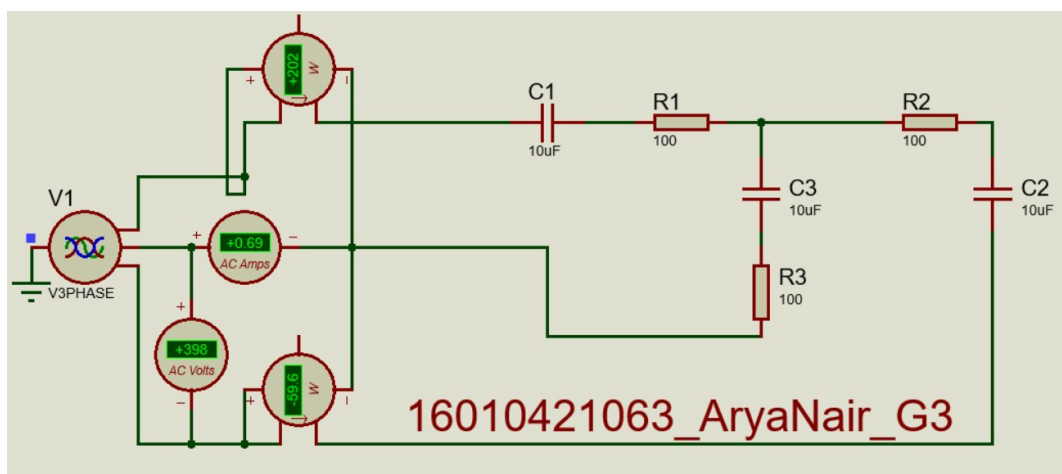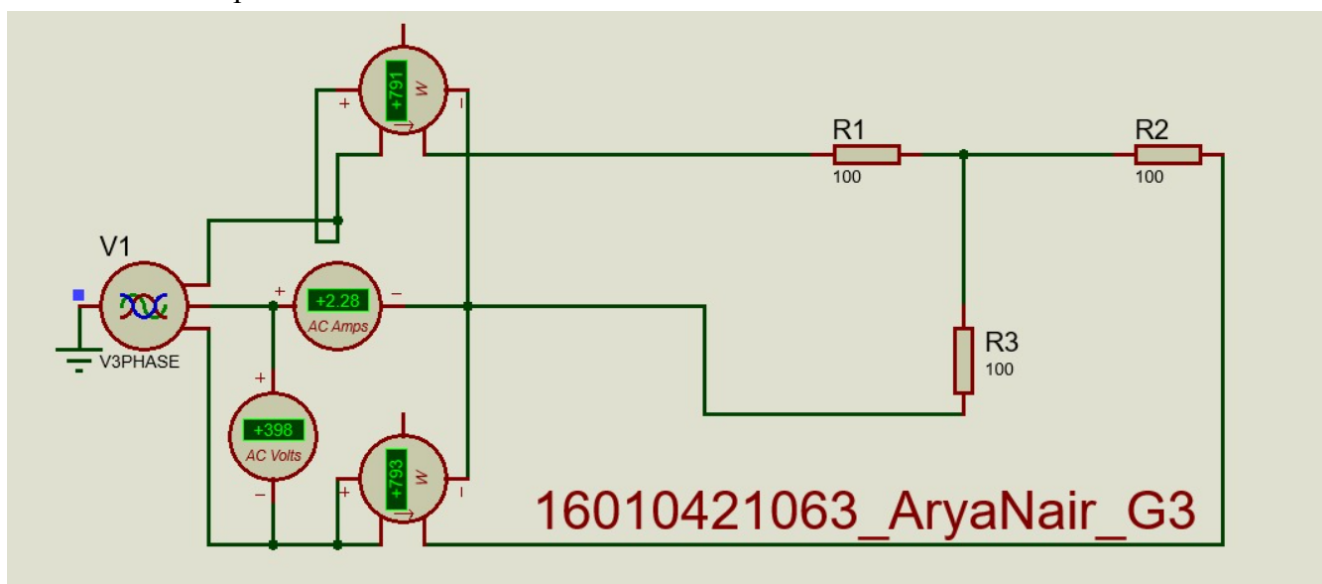

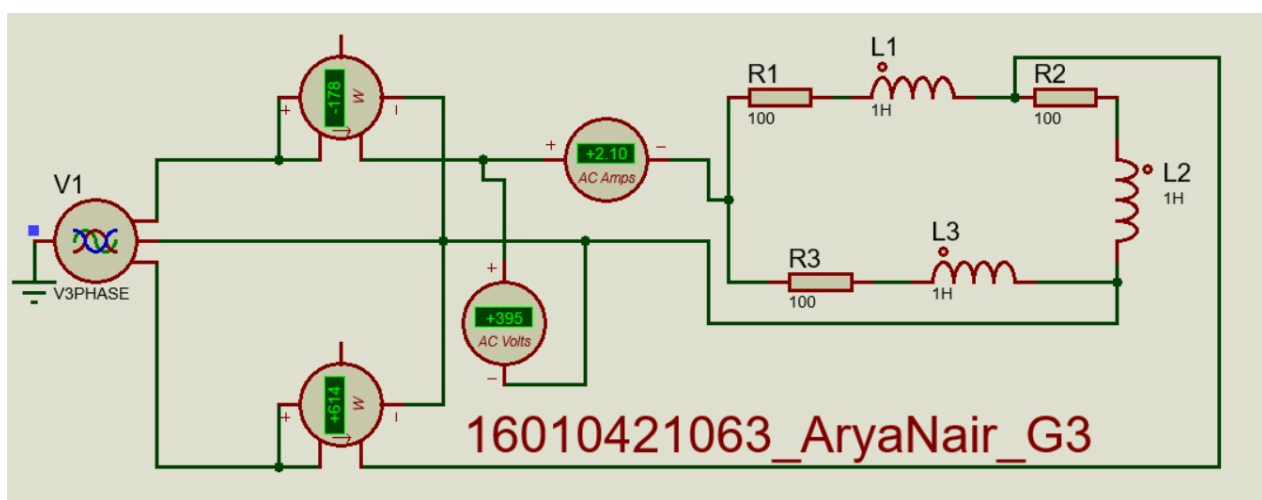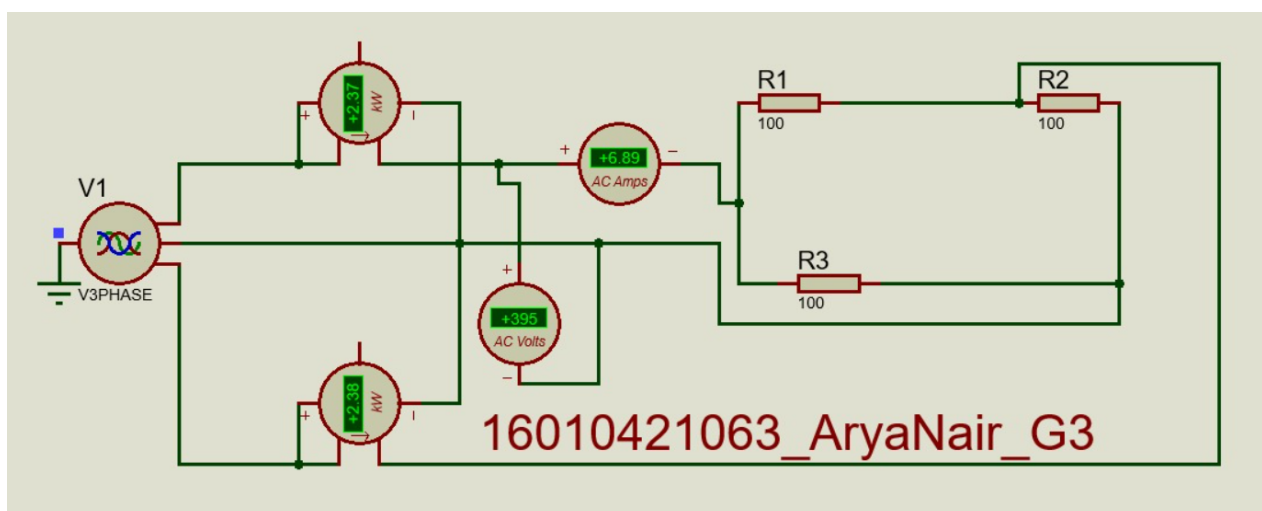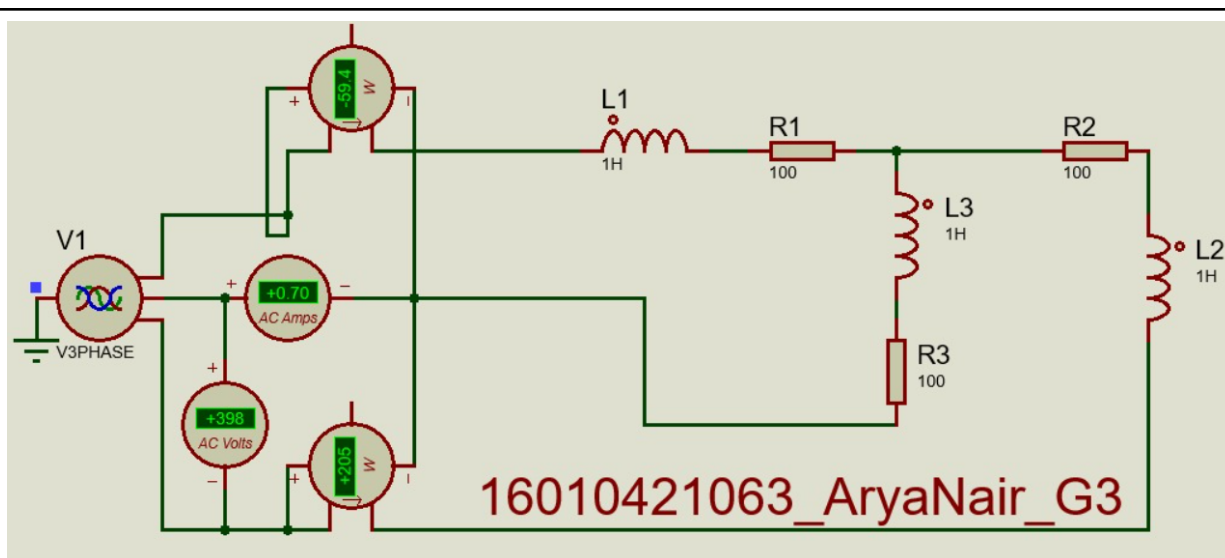

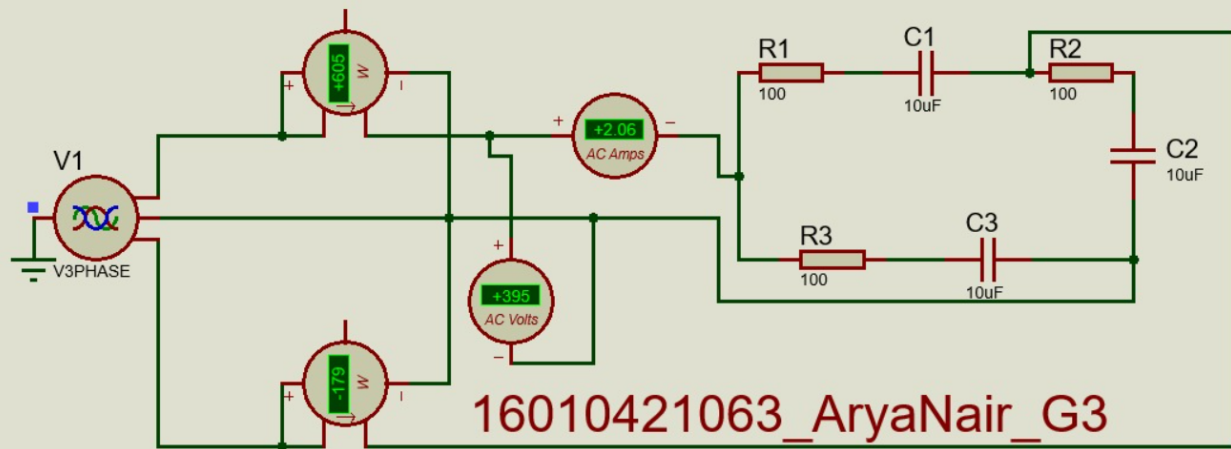

Star connected

$$W_1 = V_{RP} I_R \cos(30^\circ - \phi)$$

$$W_2 = V_{YB} I_Y \cos(30^\circ + \phi)$$

$$I_R = I_Y = I_L$$

$$V_{RB} = V_{YB} = V_L$$

$$W_1 = V_L I_L \cos(30^\circ - \phi)$$

$$W_2 = V_L I_L \cos(30^\circ + \phi)$$

$$W_1 + W_2 = V_L I_L [\cos(30^\circ + \phi) + \cos(30^\circ - \phi)]$$

$$= V_L I_L 2 \cos 30^\circ \cos \phi$$

$$= \sqrt{3} V_L I_L \cos \phi$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$$

Delta connected Load

$$W_1 = V_L I_L \cos(30^\circ - \phi)$$

$$W_2 = V_L I_L \cos(30^\circ + \phi)$$

$$W_1 + W_2 = V_L I_L [\cos(30^\circ + \phi) + \cos(30^\circ - \phi)]$$

$$= V_L I_L 2 \cos 30^\circ \cos \phi$$

$$= \sqrt{3} V_L I_L \cos \phi$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$$

Conclusion:

We used two watt meters to successfully determine the power of a three phase system

Signature of faculty in-charge with Date: