

<b>Course Name:</b>	<b>Elements of Electrical and Electronics Engineering</b>	<b>Semester:</b>	<b>I/II</b>
<b>Date of Performance:</b>		<b>Batch No:</b>	<b>G3</b>
<b>Faculty Name:</b>	<b>Milind Marathe</b>	<b>Roll No:</b>	<b>16010421063</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Mark s:</b>	<b>/ 25</b>

### Experiment No: 3

#### Title: Thevenin's Theorem & Norton's Theorem.

##### Aim and Objective of the Experiment:

- To Verify for Thevenin's Theorem for the circuit
- To Verify Norton Theorem for the Circuit.


##### COs to be achieved:

**CO1:** Analyze resistive networks excited by DC sources using various network theorems. .


##### Circuit Diagram/ Block Diagram:

###### Circuit Diagram


###### Task 1: Circuit Diagram to measure $V_{Th}$ :

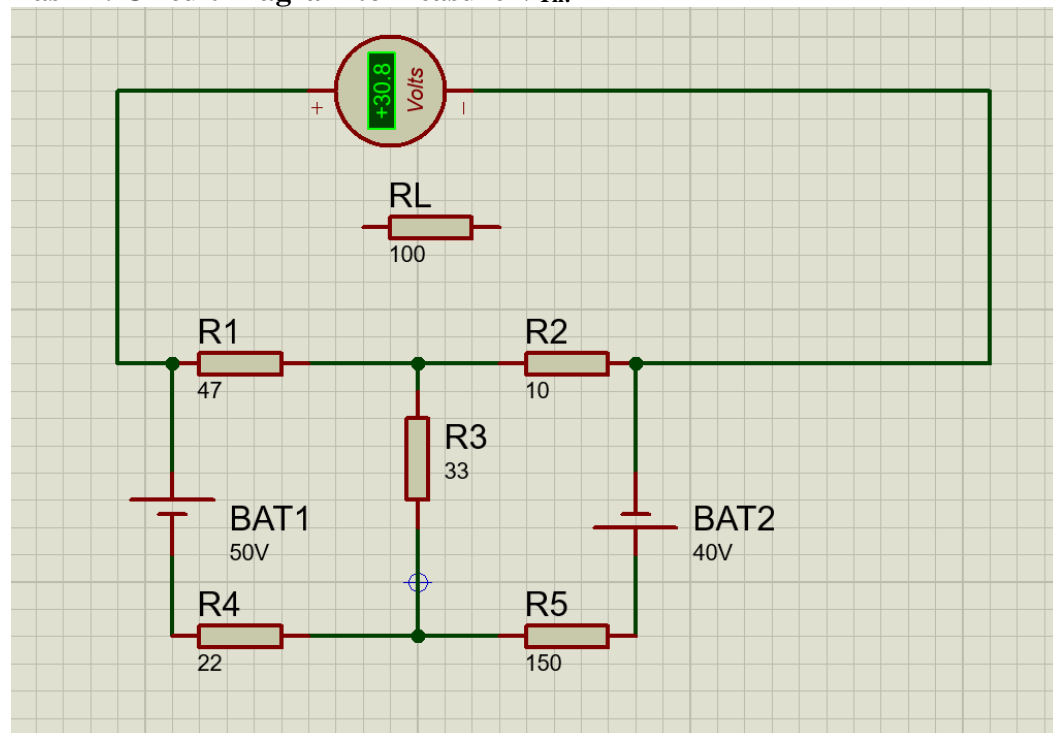

**Task 2: Circuit Diagram to measure  $I_{sc}=I_N$ :**

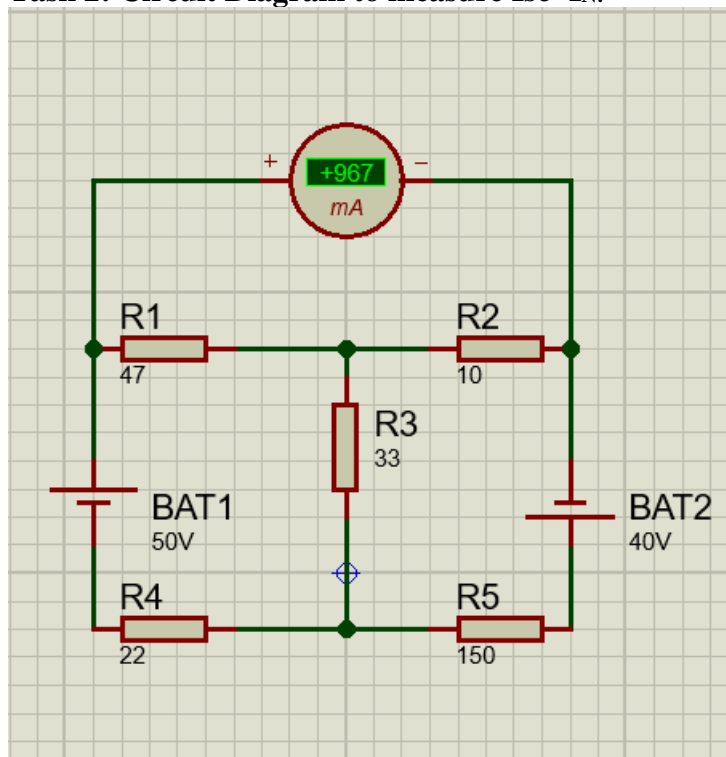

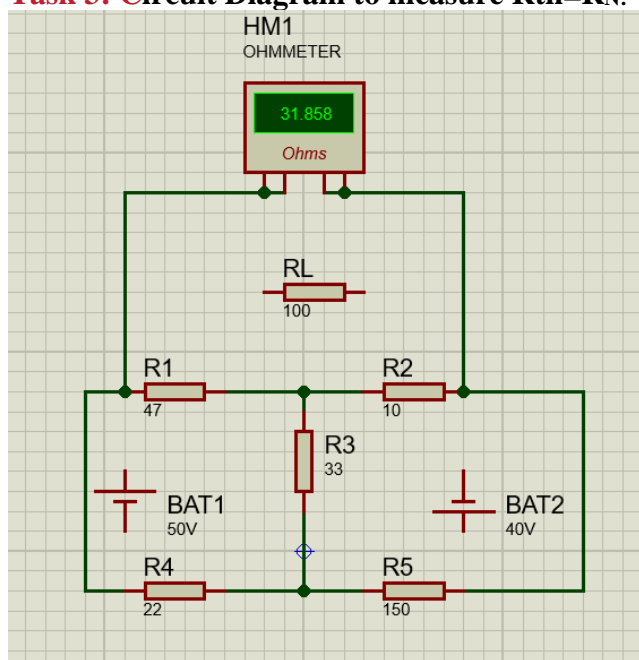**Task 3: Circuit Diagram to measure  $R_{th}=R_N$ :**



**Stepwise-Procedure:**

**Thevenin's Theorm**

1. Connect the circuit as shown in the circuit diagram.
2. Set  $V_1$ ,  $V_2$  and measure open circuit voltage  $V_{Th}$  across load terminals A and B.
3. Replace all voltage sources by Short circuit and measure  $R_{Th}$  across terminals A and B as per the circuit diagram shown in the figure.
4. Draw Thevenin's equivalent circuit and determine the value of load current from it.
5. Verify the results theoretically.

**Norton's Theorem**


1. Connect the circuit as shown in the circuit diagram.
2. Set the voltages  $V_1$ ,  $V_2$
3. Remove the load resistance and measure the short circuit current  $I_{SC}$  through A and B terminals.
4. Replace all the voltage sources by Short circuit and measure  $R_{Th}$  across terminals A and B as per the circuit diagram shown in the figure.
5. Draw Norton's equivalent circuit and determine the value of load current.
6. Verify the results theoretically

**Observation Table:**


	<b><math>I_{RL}</math></b>
<b>Practical value</b>	<b>0.23A</b>
<b>Theoretical value</b>	<b>0.23A</b>

	<b><math>V_{th}</math></b>	<b><math>R_{th} (\Omega)</math></b>	<b><math>I_{sc} (I_N)</math></b>	<b><math>I_{rl}</math> Thevenin</b>	<b><math>I_{rl} \Omega_{Norton}</math></b>
<b>Practical value</b>	<b>30.8</b>	<b>31.858</b>	<b>0.967A</b>	<b>0.23A</b>	<b>0.234A</b>
<b>Theoretical value</b>	<b>30.805</b>	<b>31.857</b>	<b>0.9669A</b>	<b>0.2336A</b>	<b>0.2343A</b>

### Thevenin's equivalent circuit

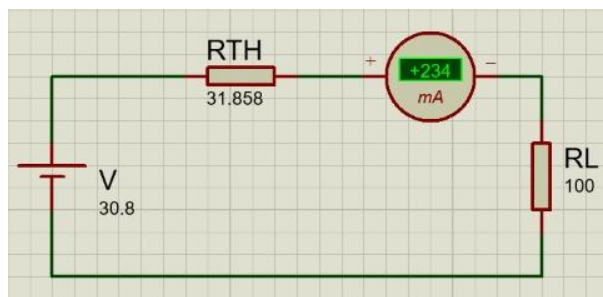


### Norton's Equivalent Circuit

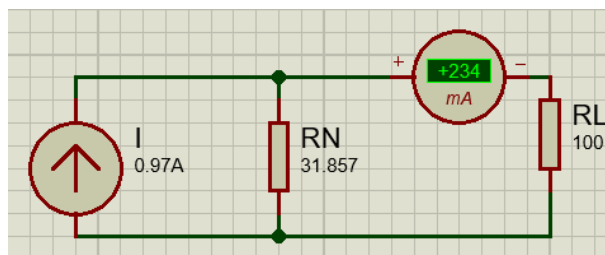

Theoretical Calculation:

$V_{th}$ :

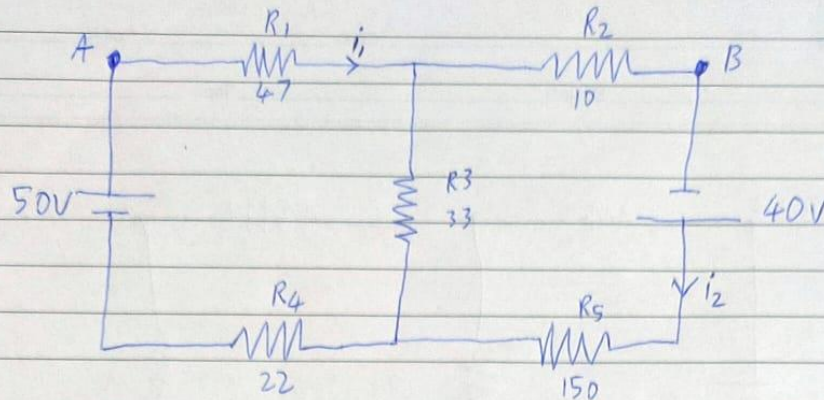

$$50 = i_1(47+22) + 33(i_1 - i_2)$$

$$50 = 69i_1 + 33i_1 - 33i_2$$

$$50 = 102i_1 - 33i_2 \quad \text{--- (1)}$$

$$40 = i_2(150+10) + (i_2 - i_1)33$$

$$= 160i_2 + 33i_2 - 33i_1$$

$$= 193i_2 - 33i_1 \quad \text{--- (2)}$$

Solving (1) and (2)

$$i_1 = 0.58988$$

$$i_2 = 0.30811$$

$$V_{TH} = V_{AB} = i_1 R_1 + i_2 R_2$$


$$= 0.58988 \times 47 + 0.30811 \times 10$$

$$= 27.72346 + 3.0811$$

$$V_{TH} = 30.80546$$



R<sub>th</sub>:

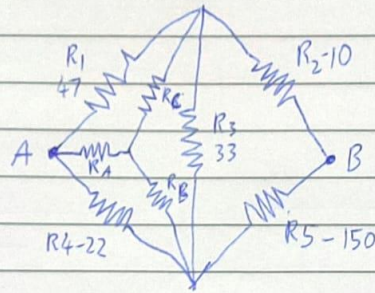

$$R_A = \frac{47 \times 22}{102} = \frac{1034}{102}$$


$$R_B = \frac{22 \times 33}{102} = \frac{726}{102}$$

$$R_3 = \frac{1551}{102}$$

$$R_A = 10.137$$

$$R_2 = 7.117$$

$$R_3 = 15.205$$

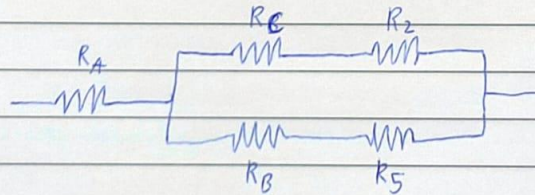

$$R_x = R_C + R_2 = 157.117$$

$$R_y = R_B + R_5 = 25.205$$

$$R_{xy} = \frac{157.117 \times 25.205}{(157.117 + 25.205)} = 21.7205$$

$$R_{TH} = 10.137 + 21.7205$$

$$R_{TH} = 31.857 \Omega$$

$I_{sc}$ :

$$I_{sc} = \frac{V_{TH}}{R_{TH}}$$

$$= \frac{30.805}{31.857}$$


$$I_{sc} = 0.9669 \text{ A}$$

$I_{RL}(\text{Norton})$ :


$$(I_{RL})100 = (0.97 - I_{RL})31.857$$

$$100I_{RL} = 30.9029 - 31.857I_{RL}$$

$$131.857I_{RL} = 30.9029$$
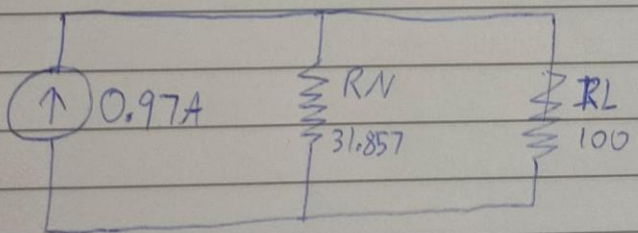
$$I_{RL} = 0.23434$$


**$I_{RL}(\text{Thevenin})$ :**

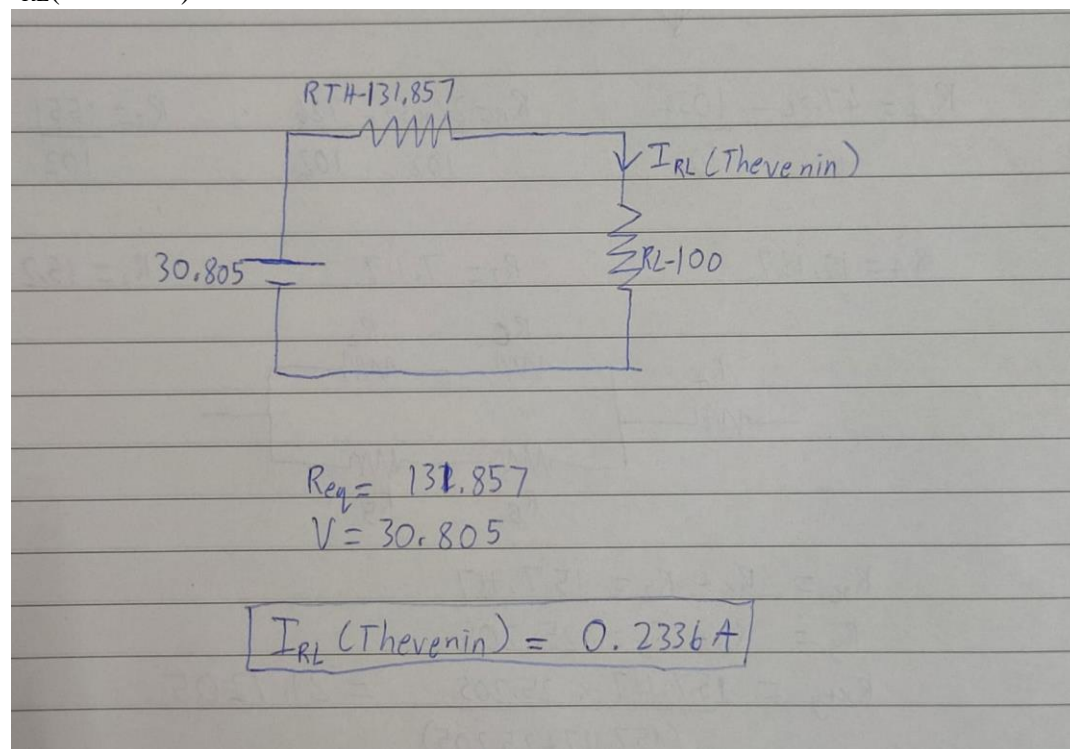

**Conclusion:**

In this experiment we understand the use of Thevenin and Norton's theorem to get the value of  $I_{RL}$  in the circuit.

**Signature of faculty in-charge with Date:**