

**Name:** Rahul Dandona**Batch:** G1**Roll No:** 16010421015

## **Experiment No. 9 – Inverting and Non-Inverting Amplifier using OPAMP**

### **Aim and Objective of the Experiment:**


- To understand the open loop configuration of OPAMP
- To understand the concept of negative feedback and closed loop configuration of OPAMP.
- To understand inverting and Non-inverting amplifier of OPAMP
- To find gain of inverting and non-inverting amplifiers


### **COs to be achieved:**

**CO5:** Understand operational amplifier and its applications


### **Circuit Diagram:**
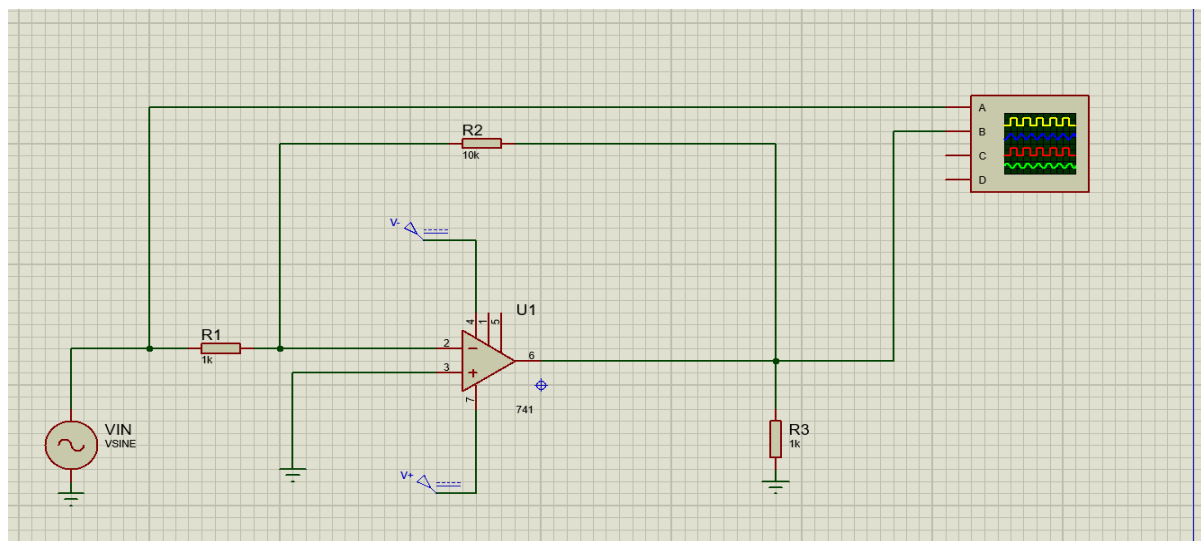
#### **1.A Inverting Amplifier: AC Input Voltage**





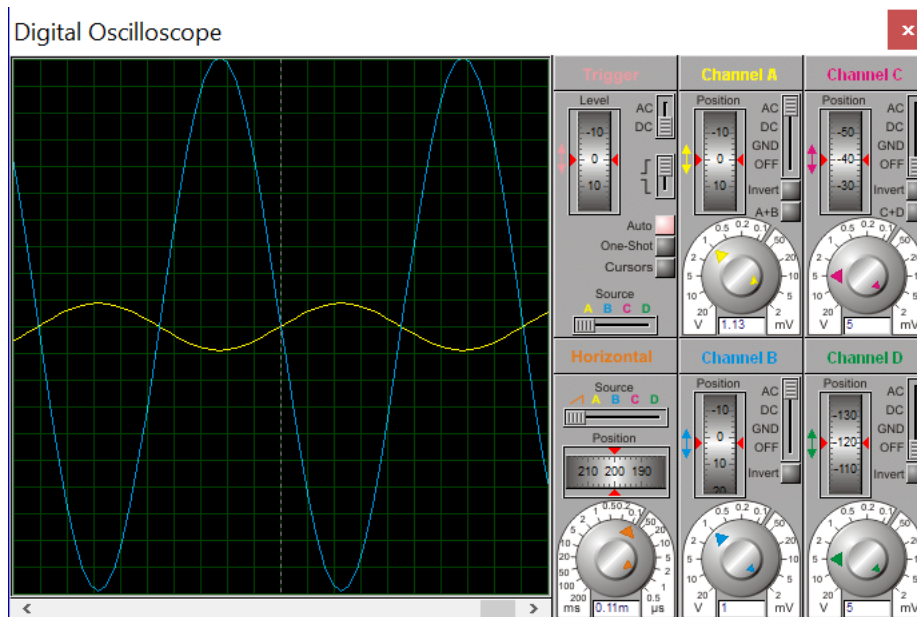

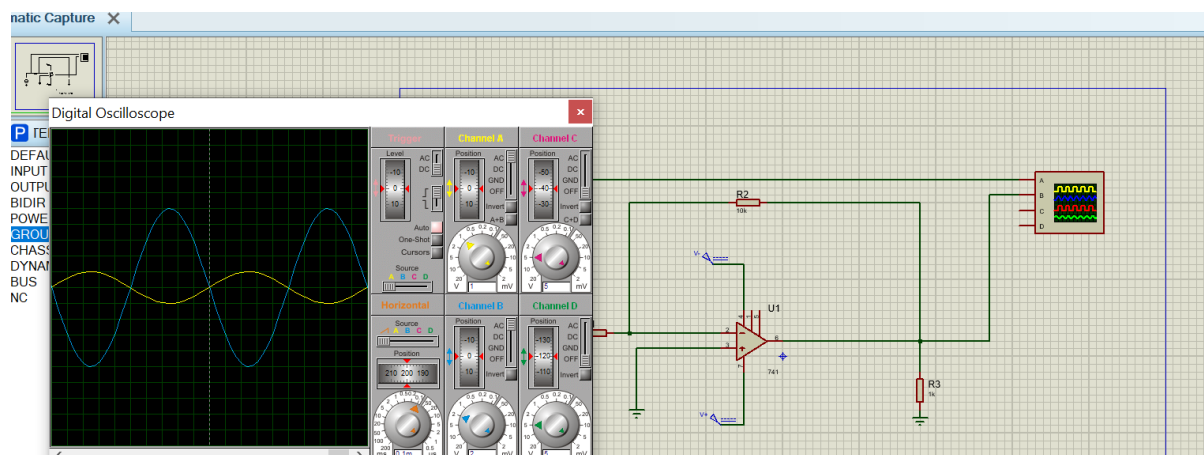
### 1.B Non-Inverting Amplifier: AC Input Voltage



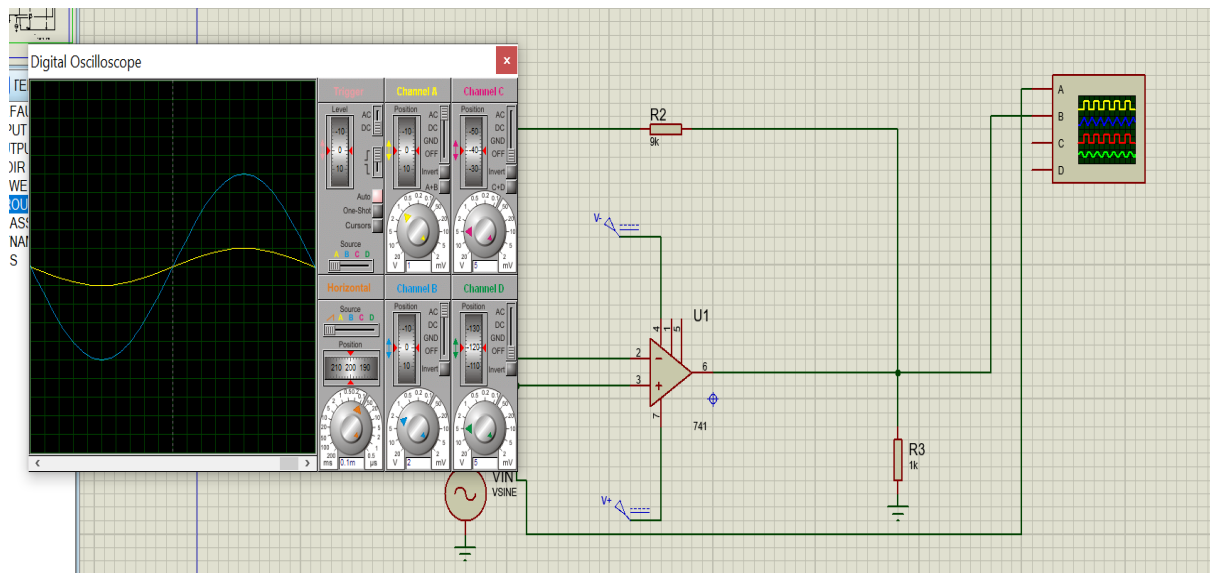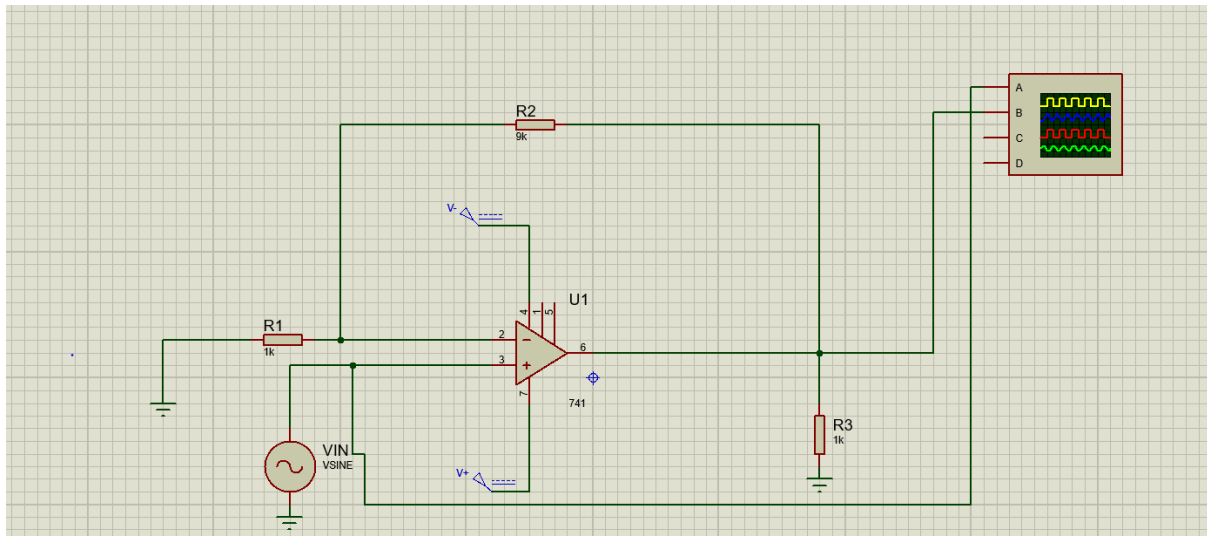
### 2.A Inverting Amplifier: DC Input Voltage


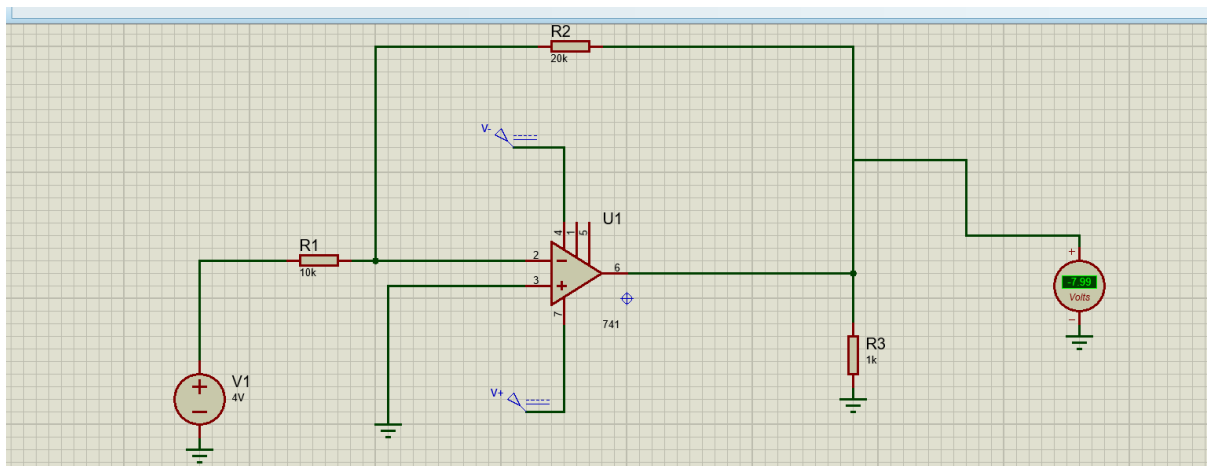
## 2.B Non-Inverting Amplifier: DC Input Voltage



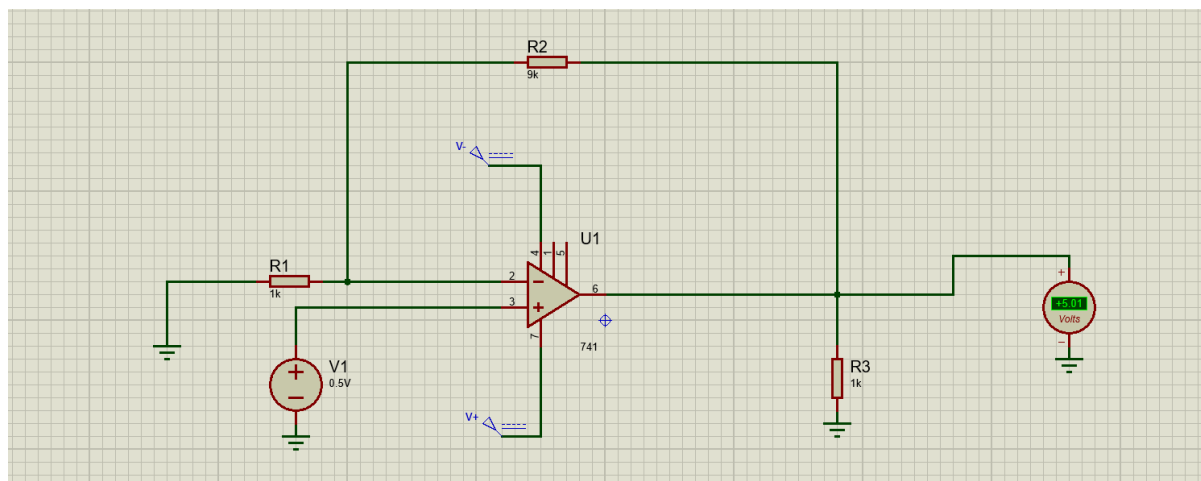

### Observation Table:

#### 1.A Inverting Amplifier: AC Input Voltage

Sr.No.	Frequency(Hz)	$V_{in}(p-p)(V)$	$V_{out}(p-p)(V)$	Practical Gain: $V_{out} / V_{in}$	Theoretical Gain: $-R_F / R_1$
1.	1000 Hz	1 Vp-p	-10 Vp-p	-10	-10
2.	1000 Hz	2 Vp-p	-20 Vp-p	-10	-10
3.	1000 Hz	4 Vp-p	-8 Vp-p	-2	-2

#### 1.B Non-Inverting Amplifier: AC Input Voltage

Sr.No.	Frequency(Hz)	$V_{in}(p-p)(V)$	$V_{out}(p-p)(V)$	Practical Gain: $V_{out} / V_{in}$	Theoretical Gain: $1 + R_F / R_1$
1.	500 Hz	1/2 Vp-p	5.5	11	11
2.	500 Hz	1 Vp-p	11	11	11
3.	1000 Hz	1 Vp-p	11	11	11

#### 2.A Inverting Amplifier: DC Input Voltage

Sr.No.	$V_{in}(p-p)(V)$	$V_{out}(p-p)(V)$	Practical Gain: $V_{out} / V_{in}$	Theoretical Gain: $-R_F / R_1$
1.	1 Vp-p	-9.99	-9.99	-10
2.	2 Vp-p	-9.99	-4.995	-5

3.	4 Vp-p	-8	-2	-2
----	--------	----	----	----

**2.B Non-Inverting Amplifier: DC Input Voltage**

Sr.No.	$V_{in}(p-p)(V)$	$V_{out}(p-p)(V)$	Practical Gain: $V_{out} / V_{in}$	Theoretical Gain: $1 + R_F / R_1$
1.	1/2 Vp-p	5.51	11.02	11
2.	1 Vp-p	11	11	11
3.	1 Vp-p	11	11	11

**Post Lab Questions:**

Experiment 9: Inverting and Non-Inverting Amplifier using OPAMP.

Q1) List the characteristics of Ideal operational amplifier.

An ideal operational amplifier is usually considered to have the following characteristics:

- Infinite open-loop gain  $G = V_{out} / V_{in}$
- Infinite input impedance  $R_{in}$ , and so zero input current.
- zero input offset voltage
- Infinite output voltage range
- zero noise
- zero output impedance  $R_{out}$ , and so infinite output current range.

Q2) List the important parameters of IC 741 operational amplifier.

The important parameters of IC 741 along with their values are as listed below:

- Differential input Resistance :  $2M\Omega$
- Input capacitance :  $1-4pF$
- output resistance :  $75\Omega$
- Input voltage Range :  $\pm 12$  to  $\pm 13V$
- Power consumption :  $85mW$
- open loop voltage Gain :  $200,000$
- output voltage swing :  $\pm 13V$  to  $\pm 15V$
- CMRR :  $90dB$